

VERILOG HDL


ModelSim-Altera 6.6d (Quartus II 11.0sp1) Starter Edition



Author: Inaam Ahmed

July 2014

 Experiment#01: Ripple Carry Counter implementation in verilog



Verilog Code

```
module ripple_carry_counter(q,clock,reset);
```

```
    output [3:0]q;
```

```
    input clock,reset;
```

```
    T_FF tff0(q[0],clock,reset);
```

```
    T_FF tff1(q[1],q[0],reset);
```

```
    T_FF tff2(q[2],q[1],reset);
```

```
    T_FF tff3(q[3],q[2],reset);
```

```
endmodule
```

```
module T_FF(q,clock,reset);
```

```
    output q;
```

```
    input clock,reset;
```

```
    wire d;
```

```
    not (d,q);
```

```
    D_FF dff(q,d,clock,reset);
```

```
endmodule
```

```
module D_FF(q,d,clock,reset);
```

```
    output q;
```

```
    input d,clock,reset;
```

```
    reg q;
```

```
always @(posedge reset or negedge clock)
```

```
if (reset)
```

```
q <= 1'b0;
```

```
else
```

```
q <= d;
```

```
endmodule
```

```
module stimulus;
```

```
reg clock;
```

```
reg reset;
```

```
wire [3:0] q;
```

```
ripple_carry_counter R(q,clock,reset);
```

```
initial
```

```
clock=1'b0;
```

```
always
```

```
#5 clock=~clock;
```

```
initial
```

```
begin
```

```
reset = 1'b1;
```

```
#15 reset = 1'b0;
```

```
#180 reset = 1'b1;
```

```
#10 reset = 1'b0;
```

```
#20 $finish;
```


```
end
```

```
initial
```


```
$monitor($time,"Output q=%d",q);
```

```
endmodule
```

Simulation Results

 

 Experiment#02 SR-Latch implementation in Verilog




Verilog Code

```
module SR_latch(q,qbar,set,reset);
    output q,qbar;
    input set,reset;
    nand(q,qbar,set);
    nand(qbar,q,reset);
endmodule
```

```
module top;
    wire q,qbar;
    reg set,reset;
    SR_latch sr1(q,qbar,{~set},{~reset});
    initial
    begin
        $monitor($time,"set=%b,reset=%b,q=%b\n",set,reset,q);
        set=0;reset=0;
        #10 reset=1;
        #10 reset=0;
        #10 set=1;
    end
```


```
endmodule
```

Simulation Results

 

Experiment#03 4_1 Mux using Gate Level Abstraction

- Behavioral Modeling

 

Verilog Code

```
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);
output out;
input i0, i1, i2, i3;
input s1, s0;
```


```

wire s1n, s0n;
wire y0, y1, y2, y3;
not (s1n, s1);
not (s0n, s0);
and (y0, i0, s1n, s0n);
and (y1, i1, s1n, s0);
and (y2, i2, s1, s0n);
and (y3, i3, s1, s0);
or (out, y0, y1, y2, y3);
endmodule

module stimulus;
reg IN0, IN1, IN2, IN3;
reg S1, S0;
wire OUTPUT;
mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
initial
begin
IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
$monitor("IN0= %b, IN1= %b, IN2= %b, IN3= %b, S0= %b, S1= %b\n",IN0,IN1,IN2,IN3,S0,S1);
S1 = 0; S0 = 0;
#10 S1 = 0; S0 = 1;
#10 S1 = 1; S0 = 0;
#10 S1 = 1; S0 = 1;
end
endmodule

```

Simulation Results

 


Experiment#04 4_1 Mux Data Flow Level

Using logic Equation

```
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);
    output out;
    input i0, i1, i2, i3;
    input s1, s0;
    assign out = (~s1 & ~s0 & i0)|
                (~s1 & s0 & i1) |
                (s1 & ~s0 & i2) |
                (s1 & s0 & i3);
endmodule

module data_flow_mux;
    reg IN0, IN1, IN2, IN3;
    reg S1, S0;
    wire OUTPUT;
    mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
    initial
        begin
            IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
            $monitor("IN0= %b, IN1= %b, IN2= %b, IN3= %b, S0= %b, S1= %b\n",IN0,IN1,IN2,IN3,S0,S1);
            S1 = 0; S0 = 0;
            #10 S1 = 0; S0 = 1;
            #10 S1 = 1; S0 = 0;
            #10 S1 = 1; S0 = 1;
        end
endmodule
```

Simulation Results

 

Using Conditional Operator

```
module multiplexer4_to_1 (out, i0, i1, i2, i3, s1, s0);
```


```

output out;
input i0, i1, i2, i3;
input s1, s0;
assign out = s1 ? ( s0 ? i3 : i2 ) : (s0 ? i1 : i0) ;
endmodule

module data_flow_mux1;
reg IN0, IN1, IN2, IN3;
reg S1, S0;
wire OUTPUT;
mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
initial
begin
IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
$monitor("IN0= %b, IN1= %b, IN2= %b, IN3= %b, S0= %b, S1= %b\n",IN0,IN1,IN2,IN3,S0,S1);
S1 = 0; S0 = 0;
#10 S1 = 0; S0 = 1;
#10 S1 = 1; S0 = 0;
#10 S1 = 1; S0 = 1;
end
endmodule

```

Simulation Results

 


Experiment#05 4_1 MUX Behavioral Modeling



```
module mux4_to_1_behavioral(out, i0, i1, i2, i3, s1, s0);
    output out;
    input i0, i1, i2, i3;
    input s1, s0;
    reg out;
    always @(s1 or s0 or i0 or i1 or i2 or i3)
    begin
        case ({s1, s0})
            2'b00: out = i0;
            2'b01: out = i1;
            2'b10: out = i2;
            2'b11: out = i3;
            default: out = 1'bx;
        endcase
    end
endmodule

module behavioral_mux;
    reg IN0, IN1, IN2, IN3;
    reg S1, S0;
    wire OUTPUT;
    mux4_to_1_behavioral mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
    initial
    begin
        IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
        $monitor("IN0= %b, IN1= %b, IN2= %b, IN3= %b, S0= %b, S1= %b\n",IN0,IN1,IN2,IN3,S0,S1);
        S1 = 0; S0 = 0;
        #10 S1 = 0; S0 = 1;
        #10 S1 = 1; S0 = 0;
        #10 S1 = 1; S0 = 1;
    end
endmodule
```

Simulation Results

 

  Experiment#06 4-bit Ripple Carry Full Adder



Verilog Code

```
module fulladd(sum, c_out, a, b, c_in);
output sum, c_out;
input a, b, c_in;
wire s1, c1, c2;
xor (s1, a, b);
and (c1, a, b);
xor (sum, s1, c_in);
and (c2, s1, c_in);
xor (c_out, c2, c1);
endmodule

module fulladd4(sum, c_out, a, b, c_in);
output [3:0] sum;
output c_out;
input[3:0] a, b;
```

```

input c_in;
wire c1, c2, c3;
fulladd fa0(sum[0], c1, a[0], b[0], c_in);
fulladd fa1(sum[1], c2, a[1], b[1], c1);
fulladd fa2(sum[2], c3, a[2], b[2], c2);
fulladd fa3(sum[3], c_out, a[3], b[3], c3);
endmodule

module stimuluso;
reg [3:0] A, B;
reg C_IN;
wire [3:0] SUM;
wire C_OUT;
fulladd4 FA1_4(SUM, C_OUT, A, B, C_IN);


initial
begin
$monitor($time, " A= %b, B=%b, C_IN= %b, --- C_OUT= %b, SUM= %b\n",
A, B, C_IN, C_OUT, SUM);
end

initial
begin
A = 4'd0; B = 4'd0; C_IN = 1'b0;
#5 A = 4'd3; B = 4'd4;
#5 A = 4'd2; B = 4'd5;
#5 A = 4'd9; B = 4'd9;
#5 A = 4'd10; B = 4'd15;
#5 A = 4'd10; B = 4'd5; C_IN = 1'b1;
end


endmodule

```

Simulation Results

 

 Experiment#07 Gate Delays Implementation in Verilog



Verilog code


```
module delay (out,a,b,c);
    output out;
    input a,b,c;
    wire e;
    and #(5) delayed_and(e,a,b);
    or #(4) delayed_or(out,e,c);
endmodule
```

```
module delayed;
    reg a,b,c;
    wire out;

    delay my_gates(out,a,b,c);

    initial
    begin
        a=1'b0;b=1'b0;c=1'b0;
        #10 a=1'b1;b=1'b1;c=1'b1;
        #10 a=1'b1;b=1'b0;c=1'b0;
        #20 $finish;
    end
endmodule
```

Simulation Results

 

Experiment#08 Hierarchical Modeling Concepts

How to create modules

// interaction with Verilog

```
module mem;  
endmodule
```

```
odule sc;  
endmodule
```

```
module xbar;  
endmodule
```

How to instantiate modules(Objects)

```
module mem;
```

```
endmodule
```

```
module sc;
```

```
endmodule
```

```
module xbar;
```

```
endmodule
```

```
module is;
```

```
mem mem1;
```

```
sc sc1;
```

```
xbar xbar1;
```

```
endmodule
```

```
module top;
```

```
is is1;
```

```
endmodule
```

Example of Ripple Adder

```
module FA;
```

```
endmodule
```

```
module ripple_add;
```

```
FA fa_0;
```

```
FA fa_1;
```







```
FA fa_2;
```

```
FA fa_3;
```

```
endmodule
```

Experiment#09 Implementation of

      - AND gate using NAND gate
- OR gate using NAND gate
- NOT gate using NAND



Verilog code

```
module my_gates(out_and,out_or,out_not,a,b);
```

```
    output out_and,out_or,out_not;
```

```
    input a,b;
```

```
//my_or
```

```
    wire x,y;
```

```
    nand(x,a,a);
```

```
    nand(y,b,b);
```

```
    nand(out_or,x,y);
```

```
//my_and
```

```
    wire z;
```

```
    nand(z,a,b);
```

```
    nand(out_and,z,z);
```

```
//my_not
```

```
    nand(out_not,a,a);
```

```
endmodule
```

```
module my_gates_top;
```


```

reg a,b;
wire out_and,out_or,out_not;
initial
begin
  a=1'b0;b=1'b0;
#10 a=1'b0;b=1'b1;
#10 a=1'b1;b=1'b0;
#10 a=1'b1;b=1'b1;
#10 $finish;
end


my_gates inst(out_and,out_or,out_not,a,b);
initial
begin
$monitor($time,"a=%b,b=%b---AND=%b---OR=%b---NOT=%b",a,b,out_and,out_or,out_not);
end
endmodule

```

Verilog Simulation Results

 

 Experiment#10 XOR gate implementation in Verilog




Source Code


```
module xor_gate(out,x,y);
    output out;
    input x,y;
    wire x1,y1,o1,o2;
    not(x1,x);
    not(y1,y);
    and(o1,x,y1);
    and(o2,y,x1);
    or my_xor(out,o1,o2);
endmodule

module top_module;
    reg x,y;
    wire out;
    xor_gate xor_block(out,x,y);
    initial
    begin
        $monitor($time,"x=%b,y=%b,OUT=%b\n",x,y,out);
        x=1'b0;y=1'b0;
        #10 x=1'b0;y=1'b1;
        #10 x=1'b1;y=1'b0;
        #10 x=1'b1;y=1'b1;
    end
endmodule
```

Verilog Simulation Results

 

 Experiment#11 Full Adder Implementation in Verilog



Source Code

```
module F_A(sum,c_out,a,b,c_in);  
  
    output sum,c_out;  
  
    input a,b,c_in;  
  
    wire a,b,c_in;  
  
    wire a1,b1,c_in1,s1,s2,s3,s4;  
  
    wire c1,c2,c3;  
  
    not(a1,a);not(b1,b);not(c_in1,c_in);  
    and(s1,a,b,c_in);  
    and(s2,a1,b,c_in1);  
    and(s3,a1,b1,c_in);  
    and(s4,a,b1,c_in1);  
  
  
  
    and(c1,a,b);  
    and(c2,b,c_in);  
    and(c3,a,c_in);  
  
  
  
    or sum_1(sum,s1,s2,s3,s4);  
    or carry_1(c_out,c1,c2,c3);
```


```

endmodule


module test_fulladder;
    wire sum,c_out;
    reg a,b,c_in;
    F_A full_adder(sum,c_out,a,b,c_in);
    initial
    begin
        $monitor($time,"A=%b,B=%b,C_IN=%b---SUM=%b,C_OUT=%b",a,b,c_in,sum,c_out);
        a=1'b0;b=1'b0;c_in=1'b0;
        #10 a=1'b0;b=1'b0;c_in=1'b1;
        #10 a=1'b0;b=1'b1;c_in=1'b0;
        #10 a=1'b0;b=1'b1;c_in=1'b1;
        #10 a=1'b1;b=1'b0;c_in=1'b0;
        #10 a=1'b1;b=1'b0;c_in=1'b1;
        #10 a=1'b1;b=1'b1;c_in=1'b0;
        #10 a=1'b1;b=1'b1;c_in=1'b1;
    end
endmodule

```

Verilog Simulation Results

 

Experiment#12 RS_Latch with delay(1).

 


Verilog Source Code


```
module SR_latch(q,qbar,set,reset);
    input set,reset;
    output q,qbar;
    nor #(1)(q,reset,qbar);
    nor #(1)(qbar,set,q);
endmodule

module latch_top;
    reg s,r;
    wire Q,Qbar;
    SR_latch my_latch(.q(Q),.qbar(Qbar),.set(s),.reset(r));
    initial
    begin
        s=1'b0;r=1'b0;
        #10 s=1'b0;r=1'b1;
        #10 s=1'b1;r=1'b0;
        #10 s=1'b1;r=1'b1;
    end
endmodule
```

Verilog Simulation Results

 

 Experiment#13 2-to-1 mux using multiplexer



The delay specification for gates b1 and b2 are as follows:

	Min	Typ	Max
Rise	1	2	3
Fall	3	4	5
Turnoff	5	6	7

Verilog Source Code

```
module buf_mux (out,in0,in1,s);
    output out;
    input in0,in1,s;
    bufif1 #(1:3:5,2:4:6,3:5:7) b2(out,in1,s);
    bufif0 #(1:3:5,2:4:6,3:5:7) b1(out,in0,s);
endmodule

module buffer_mux_top;
    reg in0,in1,s;
    wire out;
    buf_mux my_mux(out,in0,in1,s);
initial
begin
$monitor($time,"IN1=%b,IN0=%b,----S=%b,OUT=%b\n",in1,in0,s,out);
in0=1'b0;in1=1'b1;
10 s=1'b1;
```


```
#10 s=1'b0;
```

```
10 $finish;
```

```
end
```

```
endmodule
```


Verilog Simulation Results

 

Experiment#14 XOR using dataflow modeling


```
module xor_gate(out,x,y);
    output out;
    input x,y;
    assign out=x^y;
endmodule
```
 
```
module stimulus_xor;
    reg x,y;
    wire out;
    xor_gate xorgate(out,x,y);
    initial
    begin
        $monitor("x=%b y=%b---out=%b",x,y,out);
        x=1'b0;y=1'b0;
        #10 x=1'b0;y=1'b1;
        #10 x=1'b1;y=1'b0;
        #10 x=1'b1;y=1'b1;
        #10 $finish;
    end
endmodule
```




Experiment#15 XNOR using dataflow modeling
 
```
module xnor_gate(out,x,y);
    output out;
    input x,y;
    assign out=x~^y;
endmodule
module stimulus_xnor;
reg x,y;
wire out;
    xnor_gate xnorgate(out,x,y);
initial
begin
    $monitor("x=%b y=%b---out=%b",x,y,out);
    x=1'b0;y=1'b0;
#10 x=1'b0;y=1'b1;
#10 x=1'b1;y=1'b0;
#10 x=1'b1;y=1'b1;
#10 $finish;
end
endmodule
```



 1:4 demux using implementation in verilog



Verilog Code

```
module demux(o1,o2,o3,o4,x,y,en,a);
```

```
output o1,o2,o3,o4;
```

```
input x,y,en,a;
```

```
wire x_not,y_not,en_not;
```

```
not(en_not,en);
```

```
not(x_not,x);
```

```
not(y_not,y);
```

```
and(o1,x_not,y_not,en_not,a);
```

```
and(o2,x_not,y,en_not,a);
```

```
and(o3,x,y_not,en_not,a);
```

```
and(o4,x,y,en_not,a);
```


```
endmodule
```

```
module stimulus;
```

```

reg x,y,en,a;
wire o1,o2,o3,o4;
demux d_m1(o1,o2,o3,o4,x,y,en,a);
initial
begin
$monitor(" En=%b, x=%b, y=%b, Input=%b----o1=%b o2=%b o3=%b o4=%b",en,x,y,a,o1,o2,o3,o4);
en=1'b1;a=1'b1;
#10 en=1'b0;
#10 x=1'b0;y=1'b0;
#10 x=1'b0;y=1'b1;
#10 x=1'b1;y=1'b0;
#10 x=1'b1;y=1'b1;
end
endmodule


```

 

Cascaded and with 6 unit delay each, output and gate is under a feedback of and gate.

```
module delayed_and(out,x,y,z);
    output out;
    input x,y,z;
    wire e;
    assign #(6) e=x&y;
    assign #(6) out=e&z;
endmodule

module delayed_and_stimulus;
    reg x,y,z;
    wire out;
    delayed_and my_delayed_and(out,x,y,z);
    initial
    begin
        $monitor("x=%b y= %b z=%b ----- out=%b ",x,y,z,out);
        x=0;y=0;z=0;
        #10 x=0;y=0;z=0;
        #10 x=0;y=0;z=1;
        #10 x=0;y=1;z=0;
        #10 x=0;y=1;z=1;
        #10 x=1;y=0;z=0;
        #10 x=1;y=0;z=1;
        #10 x=1;y=1;z=0;
        #10 x=1;y=1;z=1;
    end
endmodule
```

 

3 To 8 Decoder

```
module Decoder_3_8(o0,o1,o2,o3,o4,o5,o6,o7,x,y,z);
output o0,o1,o2,o3,o4,o5,o6,o7;
input x,y,z;
wire x_not,y_not,z_not;
assign x_not=~x;
assign y_not=~y;
assign z_not=~z;
assign o0=x_not&y_not&z_not;
assign o1=x_not&y_not&z;
assign o2=x_not&y&z_not;
assign o3=x_not&y&z;
assign o4=x&y_not&z_not;
assign o5=x&y_not&z;
assign o6=x&y&z_not;
assign o7=x&y&z;
endmodule
```

```
module Decoder_3_8_stimulus;
reg x,y,z;
wire o0,o1,o2,o3,o4,o5,o6,o7;
Decoder_3_8 my_Decoder_3_8(o0,o1,o2,o3,o4,o5,o6,o7,x,y,z);
initial
begin
$monitor("x=%b y=%b z=%b o0=%b o1=%b o2=%b o3=%b o4=%b o5=%b o6=%b o7=%b
",x,y,z,o0,o1,o2,o3,o4,o5,o6,o7);
x=1'b0;y=1'b0;z=1'b0;
#10 x=1'b0;y=1'b0;z=1'b1;
#10 x=1'b0;y=1'b1;z=1'b0;
#10 x=1'b0;y=1'b1;z=1'b1;
```

```

#10 x=1'b1;y=1'b0;z=1'b0;

#10 x=1'b1;y=1'b0;z=1'b1;


#10 x=1'b1;y=1'b1;z=1'b0;

#10 x=1'b1;y=1'b1;z=1'b1;

end

endmodule

```

 

8 To 3 Encoder

```

module Encoder_8_3(x,y,z,o0,o1,o2,o3,o4,o5,o6,o7);
    output x,y,z;
    input o0,o1,o2,o3,o4,o5,o6,o7;
    assign x=o4|o5|o6|o7;
    assign y=o2|o3|o6|o7;
    assign z=o1|o3|o5|o7;
endmodule

```

```


module Encoder_8_3_stimulus;
    reg o0,o1,o2,o3,o4,o5,o6,o7;
    wire x,y,z;
    Encoder_8_3 my_encoder(x,y,z,o0,o1,o2,o3,o4,o5,o6,o7);

```

```

initial
begin
    $monitor("x=%b y=%b z=%b o0=%b o1=%b o2=%b o3=%b o4=%b o5=%b o6=%b
o7=%b",x,y,z,o0,o1,o2,o3,o4,o5,o6,o7);
    o0=1'b1;o1=1'b0;o2=1'b0;o3=1'b0;o4=1'b0;o5=1'b0;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b1;o2=1'b0;o3=1'b0;o4=1'b0;o5=1'b0;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b0;o2=1'b1;o3=1'b0;o4=1'b0;o5=1'b0;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b0;o2=1'b0;o3=1'b1;o4=1'b0;o5=1'b0;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b0;o2=1'b0;o3=1'b0;o4=1'b1;o5=1'b0;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b0;o2=1'b0;o3=1'b0;o4=1'b0;o5=1'b1;o6=1'b0;o7=1'b0;
    #10 o0=1'b0;o1=1'b0;o2=1'b0;o3=1'b0;o4=1'b0;o5=1'b0;o6=1'b0;o7=1'b1;
    #10 $finish;
end
endmodule

```

 

1:8 Demux implementation.

```
module Demux_1_8(o0,o1,o2,o3,o4,o5,o6,o7,x,en,s0,s1,s2);
```

```

output o0,o1,o2,o3,o4,o5,o6,o7;
input x,en,s0,s1,s2;
wire en_not=~en;
wire s0_not=~s0;
wire s1_not=~s1;
wire s2_not=~s2;
assign o0 =x&en_not&s0_not&s1_not&s2_not;
assign o1 =x&en_not&s0_not&s1_not&s2;
assign o2 =x&en_not&s0_not&s1&s2_not;
assign o3 =x&en_not&s0_not&s1&s2;
assign o4 =x&en_not&s0&s1_not&s2_not;
assign o5 =x&en_not&s0&s1_not&s2;
assign o6 =x&en_not&s0&s1&s2_not;
assign o7 =x&en_not&s0&s1&s2;
endmodule

module Demux_1_8_stimulus;
reg x,en,s0,s1,s2;
wire o0,o1,o2,o3,o4,o5,o6,o7;
Demux_1_8 my_demux(o0,o1,o2,o3,o4,o5,o6,o7,x,en,s0,s1,s2);
initial
begin
$monitor("o0=%b o1=%b o2=%b o3=%b o4=%b o5=%b o6=%b o7=%b x=%b en=%b s0=%b s1=%b s2=%b
",o0,o1,o2,o3,o4,o5,o6,o7,x,en,s0,s1,s2);
x=1'b1;
en=1'b1;
#10 en=1'b0;
s2=1'b0;s1=1'b0;s0=1'b0;
#10 s2=1'b0;s1=1'b0;s0=1'b1;
#10 s2=1'b0;s1=1'b1;s0=1'b0;
#10 s2=1'b0;s1=1'b1;s0=1'b1;

```

```

#10 s2=1'b1;s1=1'b0;s0=1'b0;
#10 s2=1'b1;s1=1'b0;s0=1'b1;
#10 s2=1'b1;s1=1'b1;s0=1'b0;
#10 s2=1'b1;s1=1'b1;s0=1'b1;
end
endmodule

```

